

IDE ASSIGNMENT

NARENDRA MANIKANTA

manikantakesana0@gmail.com

IITH - Future Wireless Communications (FWC)

CONTENTS

1	Question	1
2	Answer	1
2.1	Truth Table	1
2.2	K-Map Implementation of y .	1
2.3	K-Map Implementation of $D1$	2
2.4	K-Map Implementation of $D2$	2
3	Components	2
4	Implementation	2

2.1 Truth Table

p	q	x	\bar{p}	\bar{q}	y	$D1$	$D2$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
1	0	0	0	0	0	0	0
1	0	1	0	1	1	0	1
1	1	0	x	x	x	x	x
1	1	1	x	x	x	x	x


1 Question

A sequence detector is designed to detect precisely 3 digital inputs, with overlapping sequence detectable. For the sequence (1, 0, 1) and input data (1, 1, 0, 1, 0, 0, 1, 1, 0, 1, 0, 1, 1, 0)

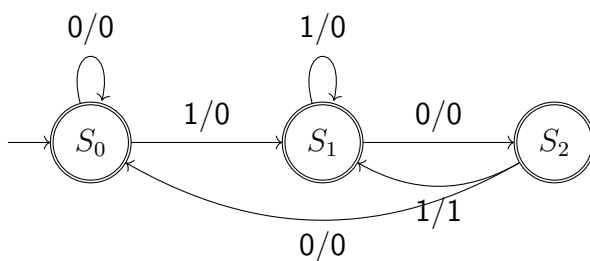- 1) 1,1,0,0,0,0,1,1,0,1,0,0
- 2) 0,1,0,0,0,0,0,1,0,1,0,0
- 3) 0,1,0,0,0,0,0,1,0,1,1,0
- 4) 0,1,0,0,0,0,0,1,0,1,0,0

2 Answer

The above question can be solved by using State diagram, Truth Table and karnaugh-map.



Truth table for Boolean function

2.2 K-Map Implementation of y

		qx			
		00	01	11	10
p	0	0	0	0	0
	1	0	1	X	X

Table. 1

herefore, the Boolean function is $y = px$.

2.3 K-Map Implementation of $D1$

		qx			
		00	01	11	10
p	0	0	0	0	1
	1	0	0	X	X

Table. 2

Therefore, the Boolean function is $D1 = q\bar{x}$.

2.4 K-Map Implementation of $D2$

		qx			
		00	01	11	10
p	0	0	1	1	0
	1	0	1	X	X

Table. 3

Therefore, the Boolean function is $D2 = x$.

3 Components

Components	Values	Quantity
Arduino	Uno	1
Jumper Wires	M-M	7
Breadboard		1
LED		2
Resistor	220 ohms	2

4 Implementation

Arduino PIN	INPUT	OUTPUT
	7	
8		LED
3		LED

Procedure

1. Connect the circuit as per the above table.
2. Upload the code for arduino from the below link.
3. verify the sequence manually fsm101
4. note: it 8 pin is reference pin and 7 pin is input and 3 pin is over output

https://github.com/arduinojinarendra/fwc_1may/blob/main/fwc/plaformio_assignment.tex